


Practice problems on Verilog (FSM)

For each problem, write Verilog code and the testbench (make sure that it works in both behavioral simulation and post-synthesis functional simulation)

Notes:

- a) the example that we did in class are on D2L: Content->Unit Verilog-> Sequential_circuits_example_Practice_problems
- b) you practiced writing Verilog code for FSM in lab 3 and lab 4

1) Write the code and testbench for

 

Note: Your circuit should also have an active-high synchronous reset (Rst).

When writing testbench, create the sequence of inputs x any y such that several cases can be shown.

For example,

Case 1: come up with x and y such that the state changes (at each clock cycle) from

SA -> SB -> SC -> SD -> SA

Case 2 (continue from case 1 in the testbench)

SA -> SB -> SB -> SC -> SC -> SA

Case 3 (continue from Case 2 in the testbench)

SA -> SC -> SC -> SD -> SA -> SC -> SA

Reminder: the purpose of the testbench is to test whether your Verilog code describes the circuit that correctly behave according to your design (state diagram).

2) Design a sequence detector, which has one input b and one output w, that accepts a sequence of bits (one bit (0 or 1) at a time) and outputs 1 when target sequences have been detected. The circuit outputs w = 1 when the previous three values of b were **110 or 101** (target sequences). **NON-overlapping** sequence is detected. Note: Your circuit should also have an active-high synchronous reset (Rst).

b 01**110101101**0100**1100**

w 0000100100100000010

When writing testbench, create sequence of b as shown above.

3) Design a synchronous sequential circuit which has an input w and an output z . The circuit outputs $z = 1$ when the previous four values of w were 1001 or 1111; otherwise $z = 0$. **Overlapping** input pattern is detected. Note: Your circuit should also have an active-high synchronous reset (Rst).

An example of the desired behavior is

w : 010111100110011111

z : 000000100100010011

When writing the testbench, create sequence of w as shown above.

4) Design a sequential circuit which has 2 inputs $w1$ and $w2$ and an output z . Its function is to compare the input sequences on the two inputs. If $w1 = w2$ during any four consecutive clock cycles, the circuit produces $z = 1$; otherwise $z = 0$.

Note: Your circuit should also have an active-high synchronous reset (Rst).

For example,

$w1$: 0110111000110


$w2$: 1110101000111

z : 0000100001110

Hint: Let $k = w1 \text{ xor } w2$ be an input to your sequential circuit \rightarrow if $w1 = w2$, $k = 0$ (based on XOR truth table).

When writing the testbench, create sequence of $w1$ and $w2$ as shown above.


5) Write the code and testbench for

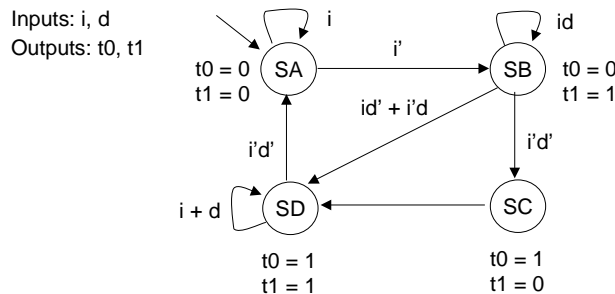

When writing testbench, create sequence of i, d to test several cases (similar idea as discussed in prob 1))

Note: Your circuit should also have an active-high synchronous reset (Rst).

6) Write the code and testbench for

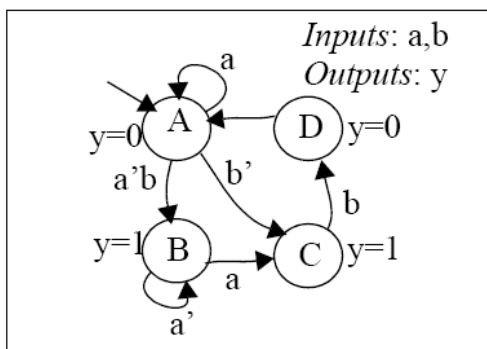

When writing testbench, create sequence of i, d to test several cases (similar idea as discussed in prob 1))

Note: Your circuit should also have an active-high synchronous reset (Rst).